

```
/dev/cu.usbmodem1411 (Arduino Uno)

voltage across at 1 3.99
voltage across at 2 0.00
voltage across 1k resistor 3.99
voltage across at 1 3.99
voltage across at 2 0.00
voltage across 1k resistor 3.99
voltage across at 1 3.99
voltage across at 2 0.00
voltage across 1k resistor 3.99
voltage across at 1 3.99
voltage across at 2 0.00
voltage across 1k resistor 3.99
voltage across at 1 3.99
voltage across at 2 0.00
voltage across 1k resistor 3.99
voltage across at 1 3.99
voltage across at 2 0.00
voltage across 1k resistor 3.99
voltage across at 1 3.99
```

Autoscroll      No line ending      9600 baud

```
/dev/cu.usbmodem1411 (Arduino Uno)

voltage across 1k resistor -3.99
voltage across at 1 0.00
voltage across at 2 3.99
voltage across 1k resistor -3.99
voltage across at 1 0.00
voltage across at 2 3.99
voltage across 1k resistor -3.99
voltage across at 1 0.00
voltage across at 2 3.99
voltage across 1k resistor -3.99
voltage across at 1 0.00
voltage across at 2 3.99
voltage across 1k resistor -3.99
voltage across at 1 0.00
voltage across at 2 3.99
voltage across 1k resistor -3.99
voltage across at 1 0.00
voltage across at 2 3.99
voltage across 1k resistor -3.99
```

Autoscroll      No line ending      9600 baud







